

Roll No.

Total Pages : 03

BT-1/D-22

41044

BASIC ELECTRICAL ENGINEERING

ES-101A


Time : Three Hours]

[Maximum Marks : 75


Note : Attempt *Five* questions in all, selecting at least *one* question from each Unit. All questions carry equal marks.

Unit I

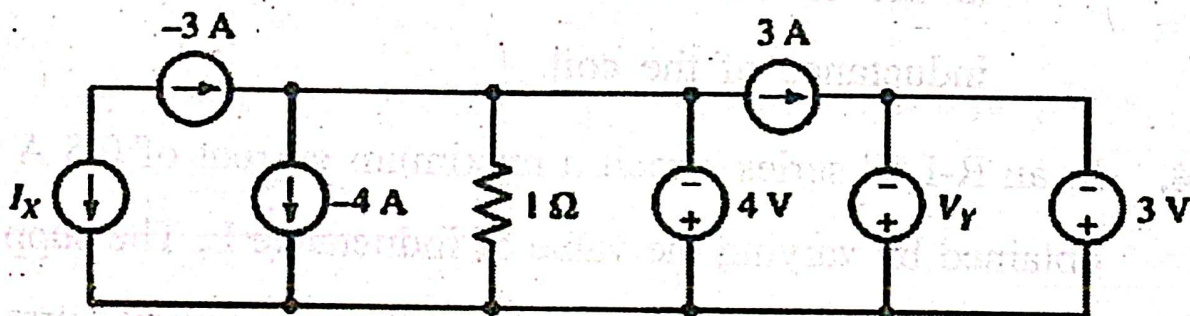1. (a) State KCL and KVL. Determine the values for I_X and V_Y in the circuit shown in figure. 8



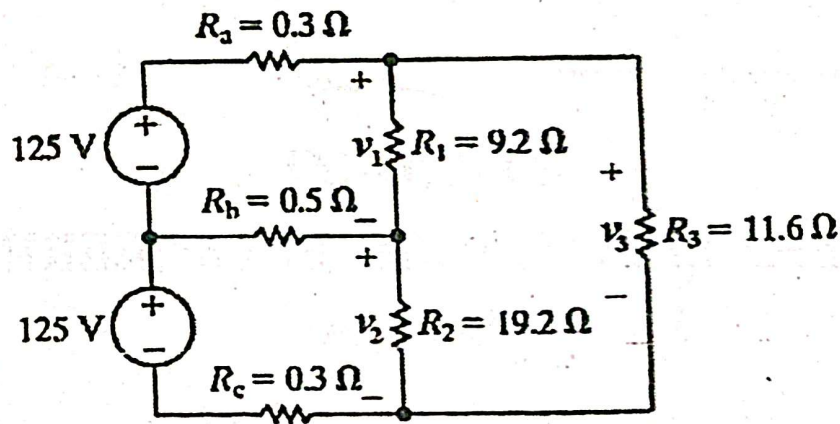- (b) State and explain superposition theorem. 7
2. (a) In the circuit shown in figure, calculate (i) v_1 , v_2 and v_3 (ii) power delivered to R_1 , R_2 and R_3 . 10



- (b) Explain Star-Delta transformation for resistors. 5

Unit II

3. (a) Explain how is the sinusoidal waveform represented as a phasor quantity with example. 7
- (b) A coil is connected in series with a capacitor of $20 \mu\text{F}$ to a 200 V variable frequency supply. The current is a maximum at 50 A, when the frequency is set to 50 Hz. Determine the resistance and inductance of the coil. 8
4. In an R-L-C series circuit a maximum current of 0.5 A is obtained by varying the value of inductance L. The supply voltage is fixed at 230 V, 50 Hz. When maximum current flows through the circuit; the voltage measured across the capacitor is 350 V. What are the values of the circuit parameters ? 15

Unit III

5. Explain the measurement of 3-phase power by two wattmeter method for a delta connected balanced load with the help of phasor diagram. 15
6. (a) From the fundamentals, derive the expression for the EMF equation of a single-phase transformer. 7
- (b) A 50 kVA, single-phase transformer has 500 turns on the primary and 200 turns on the secondary. The primary is connected to 2000 V, 50 Hz supply. Determine : (i) The secondary voltage and (ii) The maximum value of flux. 8

Unit IV

7. Explain the construction and working principle of a 3-phase Induction motor with Torque-slip characteristic. 15
8. (a) What is ELCB ? Explain the working principle of ELCB. 8
- (b) What are the different types of wires and cables ? Explain. 7