

Roll No. ....

Total Pages : 03

BT-2/M-23

42041

BASIC ELECTRICAL ENGINEERING

ES-101A

Time : Three Hours]

[Maximum Marks : 75

**Note :** Attempt *Five* questions in all, selecting at least *one* question from each Unit. All questions carry equal marks.

Unit I

1. Find Norton's equivalent of circuit shown as Fig. 1 (below), w.r.t. load resistor of  $32\Omega$ . 15

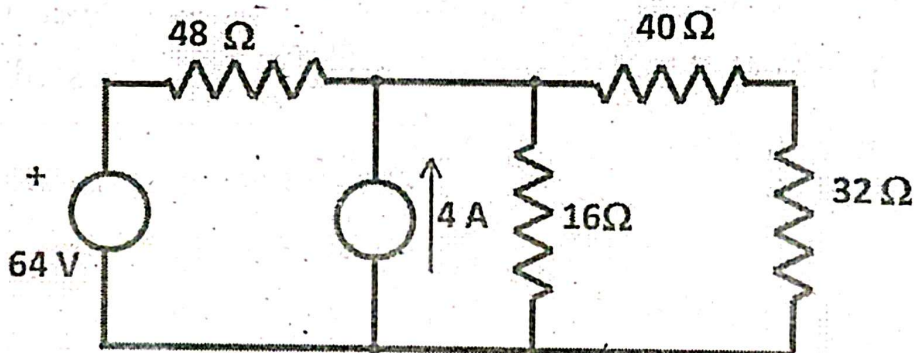


Fig. 1

2. Find Thevenin's equivalent of circuit shown as Fig. 1 (above), w.r.t. load resistor of  $16\Omega$ . 15

## Unit II

3. (a) Explain in detail the theory of sinusoidal frequency response of series RLC ckt. including resonance.

10

- (b) The voltage applied to an ac circuit is  $500\sqrt{2} \cos(100\pi t)$  V and the ckt. draws current of  $100\sqrt{2} \sin(100\pi t - 5\pi/6)$  A. Taking voltage as the reference phasor, find the phasor representation (polar form) of the current in amperes.

5

4. (a) Given the AC voltages :  $V_1 = 20 \sin(\omega t)$  V,  $V_2 = 40 \cos(\omega t)$  V and  $V_3 = -40 \cos(\omega t + 120^\circ)$  V, find their sum in periodic sine reference.

7

- (b) An ac wave  $v = V_m \sin \omega t$ , is made half wave rectified. Find the average and r.m.s. values of the new wave for complete cycle.

8

## Unit III

5. (a) Explain in detail the two wattmeter method of power measurement for a (star or delta connected) load (any type) with suitable steps containing equations, neat ckt. and phasor diagram.

10

- (b) Taking X-axis intervals of 30 degree each, draw neatly the complete waves on simultaneous axis :  
 $V_1 = V_m \sin \omega t$ ,  $V_2 = V_m \sin (\omega t - 120^\circ)$  and  
 $V_3 = V_m \sin (\omega t - 240^\circ)$ . 5
6. (a) Explain in detail the OC and SC test on a single phase transformer. 12
- (b) Deduce condition of maximum efficiency of a single phase transformer. 3

### Unit IV

7. (a) Explain in detail the construction of a DC motor and working of commutator using neat sketches. 10
- (b) Derive generated EMF equation in case of a DC generator. 5
8. (a) With neat sketches, explain and prove the statement :  
 'A 3 phase pulsating magnetic flux produced by 3-phase excited stator winding is equivalent to a single (bipolar) rotating flux'. Hence, explain how the rotor of squirrel cage type 3-phase induction motor starts rotating. Also explain slip. 12
- (b) Give function of an armature coil in an electrical machine. Give examples of motors/generators in which field is stationary/moving with respective armature moving/stationary. 3