

Roll No.

Total Pages : 03

BT-2/M-24

42041

BASIC ELECTRICAL ENGINEERING
ES-101A


Time : Three Hours]

[Maximum Marks : 75

Note : Attempt *Five* questions in all, selecting at least *one* question from each Unit.

Unit I

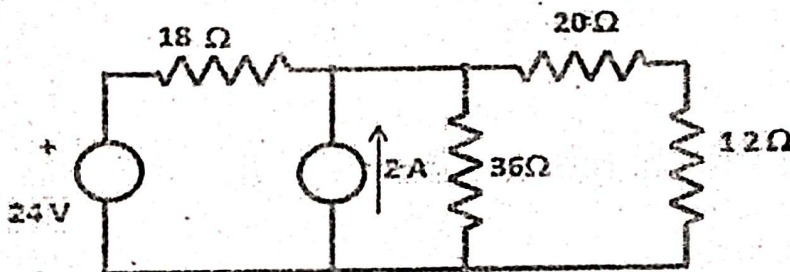1. Find Thevenin's equivalent of circuit shown as Figure-1, w.r.t. the $12\ \Omega$ resistor. 15



2. (a) Explain Maximum power transfer theorem and correlate it with Thevenin's theorem. 9
- (b) A resistor R is connected in series with a parallel circuit containing of two resistors having resistance of 12 and 8 ohm, respectively. The total power dissipated in the circuit is 96 watt and applied voltage is 24 V . Calculate the value of R . 6

Unit II

3. (a) Explain in detail the theory of sinusoidal AC response of series RC ckt. with neat sketches and waveforms. 10
- (b) Given the voltages $V_1 = 40 \sin(\omega t) V$ and $V_2 = 40 \cos(\omega t) V$, find their sum in periodic sine reference. 5
4. (a) Explain the generation of sinusoidal AC emf with the help of dynamo and neat waveforms. 10
- (b) Find the average values for full and complete cycles of an ac wave $v = V_m \sin \omega t$. 5

Unit III

5. (a) Establish relation between line voltage and phase voltage in a star connected balanced 3-phase system. 8
- (b) Taking X-axis intervals of 30 degrees each, draw neatly the complete waves on simultaneous axis :
 $V_1 = V_m \sin \omega t$, $V_2 = V_m \sin(\omega t - 120^\circ)$ and
 $V_3 = V_m \sin(\omega t - 240^\circ)$. 7
6. (a) Explain single phase actual transformer at no load. 10

- (b) Deduce condition of maximum efficiency of a single phase transformer. 5

Unit IV

7. Explain in detail the construction of a DC generator and working of commutator using neat sketches. 15
8. With neat sketches, explain and prove the statement : 'A 3 phase pulsating magnetic flux produced by 3-phase excited stator winding is equivalent to a single (bipolar) rotating flux'. Hence, explain how the rotor of squirrel cage type 3-phase induction motor starts rotating. Also explain the concept of slip. 15