

BT-3/D-21**43158****DIGITAL ELECTRONICS AND LOGIC DESIGN****Paper-ES-217 A**

Time : Three Hours]

[Maximum Marks : 75

Note : Attempt *five* questions in all, selecting at least *one* question from each unit.

UNIT-I

1. (a) Perform the following operation using 2's compliment :
45-28.
- (b) State and prove De-Morgan's theorem for Boolean algebra. Prove $A(A'+C) (A'B+C') = 0$.
- (c) Design a BCD to Gray code converter. (5×3=15)
2. (a) Discuss in brief about error detection and correction codes. 5
- (b) Minimize the following expression using K-Map and realize the obtained expression using NAND gates only :
 $F(A, B, C, D) = \sum m (0, 2, 3, 5, 7, 8, 9, 13)$. 10

UNIT-II

3. (a) Design a full adder using two half adders. 7
- (b) Explain working of 4:1 MUX. Realize the following expression using 8:1 Mux :
 $Y = \sum m (0, 1, 2, 3, 6, 7, 9, 10, 11, 12, 15)$. 8

4. (a) What is encoder ? Design and explain working of BCD to binary encoder. 7
- (b) What is demultiplexer ? How is it different from decoder? Design 1:8 demultiplexer. 8

UNIT-III

5. (a) What is flip flop? Draw logical diagram of SR flip-flop. Explain its working. Mention the problem associated with SR flip-flop. 8
- (b) Convert SR flip-flop to JK flip-flop. 7
6. (a) Design mod 6 asynchronous counter. 7
- (b) What are registers? Mention different types of registers. Explain their working. 8

UNIT-IV

7. (a) Explain working of weighted resistor D/A converter. 8
- (b) Describe the specifications of D/A converter. 7
8. (a) Draw diagram of successive approximation type A/D converter. 8
- (b) Explain working of PAL logic device. 7
-