

Roll No.

Total Pages : 03

BT-3/D-22

43146

DIGITAL ELECTRONICS

Paper : II

ES-205A

Time : Three Hours]

[Maximum Marks : 75

Note : Attempt *Five* questions in all, selecting at least *one* question from each Unit. All questions carry equal marks.

Unit I

1. (a) Express the following decimal numbers in binary form : 2
 - (i) 37
 - (ii) 255.
- (b) Perform the following operations using 2's complement : 4
 - (i) $48 - 23$
 - (ii) $23 - (-67)$.
- (c) Convert into POS term : 4
 $AB + AC' + BC$.
- (d) Design a BCD to excess 3 code converter. 5
2. (a) What are parity check codes ? Explain Hamming codes in detail. 5

- (b) Minimize the expression using Q-M method :

$$Y = \Sigma m(0, 3, 6, 7, 10, 12, 15) + d(1, 2, 9, 11).$$

Also realize the obtained expression using AOI logic.

10

Unit II

3. (a) Explain the working of TTL NAND gate. also describe the totem pole output driver circuit. 10
- (b) Explain how CMOS logic families can be interfaces with TTL families. 5
4. (a) Draw the diagram of 2-Input CMOS NAND and NOR gates. 8
- (b) Design an octal to binary encoder. 7

Unit III

5. (a) Explain in detail the working of JK flip-flop. Mention the problem associated with it. 8
- (b) Convert SR flip-flop to T flip-flop. 7
6. (a) Design a synchronous mod 10 up counter. 10
- (b) Draw and explain the working of Johnson counter. Draw the output waveforms for it. 5

Unit IV

7. (a) Write a short note on ROM. Also draw diagram showing working of ROM array. 7

(b) With the help of waveforms, explain how read and write operation occur in semiconductor memory. 8

8. Write a note on PLDs. Mention advantages of PLD. Discuss PLA and PAL. Implement the following function using PAL :

$Y = f_1 + f_2 + f_3$, where $f_1 = \Sigma m(0, 1, 2)$; $f_2 = \Sigma m(1, 2, 4)$
and $f_3 = \Sigma m(0, 3, 5)$. 15

