

BT-3/D-22

43145

ELECTRONIC DEVICES

FC-201A

Time : Three Hours]

[Maximum Marks : 75

Note : Attempt *Five* questions in all, selecting at least *one* question from each Unit.

Unit I

1. (a) Sketch an energy band diagram, and explain conduction band, valence band and forbidden gap in details. 10
- (b) Draw a diagram to illustrate drift current in a semiconductor material. Briefly explain. 5
2. (a) Describe the negative and positive shunt clipping circuits and explain the operation of each circuit. 8
- (b) Explain the current flow in a forward biased PN junction with relevant expression for minority carrier concentration and diagram to illustrate the carrier density close to depletion layer. 7

Unit II

3. (a) Draw and explain the practical transistor CE amplifier. Also explain the function of each component. 8
- (b) Explain basic principle of operation of BJT as amplifier. Also explain all the operative modes of BJT. 7
4. (a) Draw and explain H parameters of CE Transistor. 8
- (b) Give comparison of CB, CC, CE configurations. 7

Unit III

5. Explain the following terms in detail : 15
- (a) Pinch off voltage
- (b) Channel length modulation.
- (c) Velocity saturation
- (d) AC drain resistance
- (e) Amplification factor.
6. What is MOSFET ? Explain the construction and characteristics of N channel MOSFET with a suitable diagram. 15

Unit IV

7. (a) Outline the construction of Zener voltage regulator with a neat circuit diagram. 5

(b) With a neat sketch, explain the working of Op-Amp Shunt voltage regulator. 10

8. Write short notes on any *three* of the following : $5 \times 3 = 15$

- (a) Controlled Transistor shunt voltage regulator
- (b) Op Amp Series voltage Regulator
- (c) MOS capacitor
- (d) DC Regulated power supply.

