

BT-3/D-21

43157

ELECTRONICS FUNDAMENTALS

Paper : ES-201A

Time : Three Hours]

[Maximum Marks : 75

Note : Attempt *five* questions in all, selecting at least *one* question from each unit.

UNIT-I

1. (a) What is a PN junction diode? Draw and discuss the V-I characteristics of a PN junction diode.
(b) Differentiate between full wave rectifier and bridge rectifier. 15
2. (a) How a Zener diode act as a Voltage Regulator? Discuss the operation in detail.
(b) Discuss with the help of VI characteristics, how an Avalanche breakdown differs from a Zener breakdown. 15

UNIT-II

3. (a) Discuss the operation of a transistor as a switch.
(b) Discuss in detail the operation of a NPN transistor. 15

4. (a) What is biasing? Discuss in detail the Voltage divider biasing method.
- (b) Draw and explain the common emitter transistor configuration and its characteristics. 15

UNIT-III

5. (a) What is Barkhausen criterion of oscillations? Derive its equation.
- (b) What is Hartley's Oscillator? Discuss its operation in detail. 15
6. Write short notes on the following :
- (a) Colpitt's oscillator.
- (b) Wein bridge oscillator. 15

UNIT-IV

7. (a) Discuss the terms, Sensitivity, Resolution, Accuracy and Precision in context to electronic measurement system.
- (b) What is an error? Discuss the various types of errors encountered in an electronic measurement system. 15
8. (a) What is a transducer? Discuss the working of a LVDT with its applications.
- (b) What is Data acquisition system? With the help of a block diagram, explain its working. 15
-